

Contents

0.1	General Components	1
0.2	RC and RL Circuits	5
0.3	AC Circuits	6
0.3.1	AC Filters	8
0.3.2	Transformers	10
0.4	Silicon-based Components	10

0.1 General Components

Definition 0.1.1. **Electric Field** force per unit charge or N/C

Definition 0.1.2. **Voltage** or *Potential* is the change in energy per unit charge brought on by traveling through an electric field or J/C or simply V

Remark. The units N/C is equivalent to V/m

Definition 0.1.3. **Power** can be derived from units of current and voltage for the following formula where P is power(W), V is voltage(V), and I is current(A).

$$P = VI \quad (0.1.1)$$

Law 0.1.1. **Ohms Law** models the voltage drop across a purely resistive load with the following formula where V is voltage(V), I is current(A), and R is resistance(Ω).

$$V = IR \quad (0.1.2)$$

Definition 0.1.4. A **Resistor** a device that will produce a voltage drop according to ohms law with a resistance as V/A



Definition 0.1.5. **Resistivity**($\Omega \text{ m}$) is used to calculate how much resistance we expect from a material use the following formula where R is resistance(Ω), ρ is **Resistivity**($\Omega \text{ m}$), l is length(m), and A is cross sectional area(m^2).


$$R = \rho \frac{l}{A} \quad (0.1.3)$$

Law 0.1.2. **Kirchoff's Voltage Law** states precisely that the algebraic sum of all voltages around a closed path is zero.

$$\sum V_n = 0 \quad (0.1.4)$$

Law 0.1.3. **Kirchoff's Current Law** states precisely that the algebraic sum of all currents entering a node is zero.

$$\sum I_n = 0 \quad (0.1.5)$$

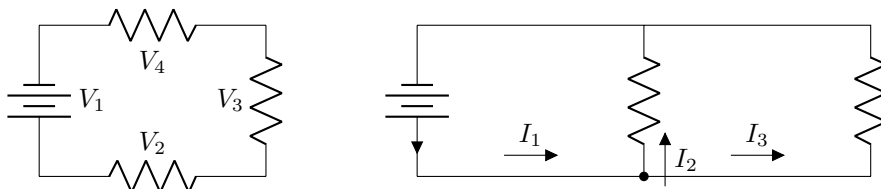


Law 0.1.4. Resistors in Series will simply be the sum of the individual resistance because we are adding the length of the resistors together.




$$R_T = \sum R_i \quad (0.1.6)$$

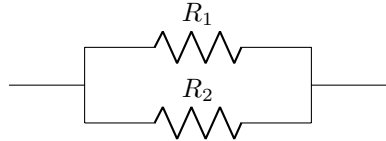Law 0.1.5. Resistors in Parallel will decrease the overall resistance as indicated by the definition of resistivity 0.1.5.



$$\frac{1}{R_T} = \sum \frac{1}{R_i} \quad (0.1.7)$$

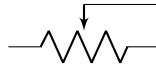Definition 0.1.6. Voltage Divider or Potentiometer is an arrangement of two resistors with a connection between them. A potentiometer refers to a voltage divider where the resistance ratio between the two resistors can be adjusted.




To calculate the voltage we expect at the divider we need to know the voltage across the whole potentiometer V and the ratio between the two resistors $\frac{R_2}{R_1}$.



$$V_{div} = V \frac{R_2}{R_1 + R_2} \quad (0.1.8)$$

Definition 0.1.7. Ideal Battery - a battery that always produces the same potential difference.

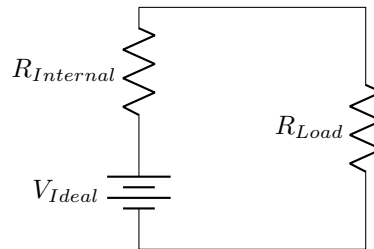Definition 0.1.8. Real Battery - a battery with some internal resistance that reduces the potential difference across the terminals depending on the amount of current.




$$V_{Real} = V_{Ideal} - IR_{Internal}$$

$$V_{Real} = V_{Ideal} \frac{R_{Load}}{R_{Internal} + R_{Load}} \quad (0.1.9)$$

Definition 0.1.9. Ideal Current Source - a device that always provides that same current to a load.

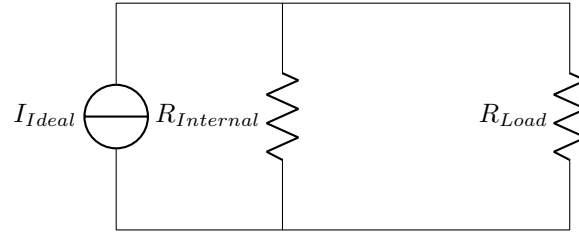Definition 0.1.10. Real Current Source - a current source with an internal resistance connected in parallel that reduces the current produced when the load resistance is high.



$$I_{Real} = I_{Ideal} - \frac{V}{R_{Internal}}$$

$$I_{Real} = I_{Ideal} \frac{R_{Internal}}{R_{Internal} + R_{Load}} \quad (0.1.10)$$

Definition 0.1.11. A Capacitor is a device that accumulates a charge q when a voltage v is applied with a proportionality constant C with units $\text{F}(\text{farad}) = \text{C V}^{-1} = \text{C}^2 \text{J}^{-1}$

$$q = Cv \quad (0.1.11)$$

$$i = C \frac{dv}{dt} \quad (0.1.12)$$



Remark. The energy stored in a capacitor can be derived by integrating power over time:

$$\omega_C = \frac{1}{2} C v^2 \quad (0.1.13)$$

Definition 0.1.12. A Plate Capacitor is a capacitor made of two conductive plates with area A separated by distance l .


$$C = \frac{\epsilon_0 \kappa A}{l}$$

Law 0.1.6. Capacitors in Series will decrease the overall capacitance.



$$\frac{1}{C_T} = \sum \frac{1}{C_i} \quad (0.1.14)$$

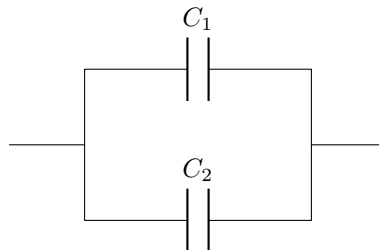Law 0.1.7. Capacitors in Parallel is simply the sum of the individual capacitance.




$$C_T = \sum C_i \quad (0.1.15)$$

Definition 0.1.13. An **Inductor** is a device which accumulates a magnetic flux $\phi = BA$ when a current is applied with a proportionality constant L with units H(henry) = J A⁻²

$$\phi = Li \quad (0.1.16)$$


$$v = L \frac{di}{dt} \quad (0.1.17)$$

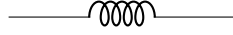

Remark. The energy stored in an inductor can be derived by integrating power over time:


$$\omega_L = \frac{1}{2} Li^2 \quad (0.1.18)$$

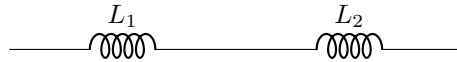Law 0.1.8. Inductors in Series is simply the sum of the individual inductance.



$$L_T = \sum L_i \quad (0.1.19)$$

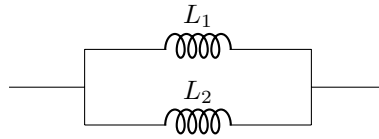Law 0.1.9. Inductors in Parallel will decrease the overall inductance.



$$\frac{1}{L_T} = \sum \frac{1}{L_i} \quad (0.1.20)$$

0.2 RC and RL Circuits

Definition 0.2.1. Charging RC Circuit is a circuit with a resistor, capacitor and voltage source to charge the capacitor. The voltage equation around the loop can be written as

$$V = Ri + \frac{1}{C} \int_0^t i(\sigma) d\sigma$$

$$i(t) = \frac{V}{R} e^{-t/RC}$$

$$v_c(t) = V(1 - e^{-t/RC})$$

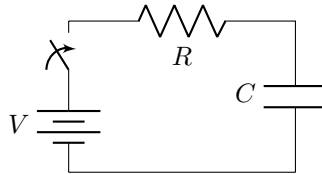


Figure 1: a basic RC circuit in the charging arrangement

Definition 0.2.2. Discharging RC Circuit is a circuit with a capacitor and resistor to discharge the capacitor. The current relation during discharge is symmetric to charge so we can rewrite the equations

$$i(t) = \frac{V}{R} (1 - e^{-t/RC})$$

$$v_c(t) = V e^{-t/RC}$$

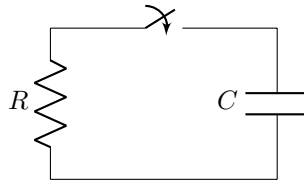


Figure 2: a basic RC circuit in the discharging arrangement

Definition 0.2.3. Charging RL Circuit is a circuit with a resistor, inductor and voltage source to charge the inductor. The current equation can be written as

$$i(t) = \frac{V}{R}(1 - e^{-tR/L})$$

$$v_L(t) = Ve^{-tR/L}$$

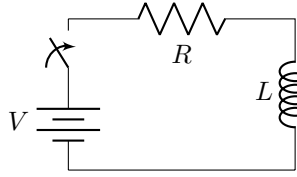


Figure 3: a basic RL circuit in the charging arrangement

Definition 0.2.4. Discharging RL Circuit is a circuit with a inductor and resistor to discharge the inductor. The current relation during discharge is symmetric to charging so we can rewrite the equations

$$i(t) = \frac{V}{R}e^{-tR/L}$$

$$v_L(t) = Ve^{-tR/L}$$

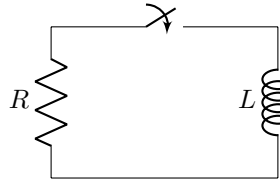


Figure 4: a basic RL circuit in the discharging arrangement

0.3 AC Circuits

Definition 0.3.1. An AC Voltage source is a voltages source with a alternating voltage. Typically the voltage changes according to the following function:

$$V(t) = V_p \sin(\omega t)$$

Definition 0.3.2. Effective Voltage or Root Mean Square Voltage is the voltage $V_p/\sqrt{2}$ where V_p is the peak sinusoidal voltage. This represents the DC voltage that would produce the same power draw as the AC voltage.

Example. Resistor in AC Circuit Bellow is a AC Circuit with a resistor. The current is determined by the following function

$$i(t) = \frac{V_p}{R} \sin \omega t$$



Figure 5: a basic AC circuit connected to a resistive load

Definition 0.3.3. Effective Current or Root Mean Square Current is the current $I_p/\sqrt{2}$ where I_p is the peak sinusoidal current. This represents the DC current that would produce the same power draw as the AC current.

Example. Capacitor in AC Circuit Bellow is a AC Circuit with a capacitor. The current is determined by the following function

$$i(t) = -\omega CV_p \sin \omega t$$

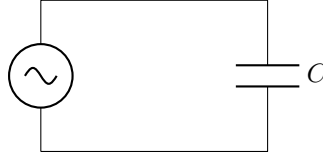


Figure 6: a basic AC circuit connected to a capacitive load

Definition 0.3.4. A Phasor Signal is a complex number that we use to represent the output of a wavelike function.

$$Re^{i\theta} = R \cos(\theta) + Ri \sin(\theta)$$

Law 0.3.1. To convert from a phasor signal to the observed signal the following formula applies where $x(t)$ is the observed signal and c is the complex phasor signal.

$$x(t) = \text{Real}(c \cdot e^{i\omega t})$$

Law 0.3.2. Generalized Ohm's Law is the complex version of ohm's law that includes complex impedance.

$$\tilde{V} = \tilde{I}\tilde{Z}$$

$$\tilde{Z} = R + iX$$


Where R is circuit resistance and X is circuit reactance.

Example. Impotence of basic components:

- **Resistor** $\tilde{Z} = \frac{\tilde{V}}{\tilde{I}} = R$
- **Capacitor** $\tilde{Z} = \frac{\tilde{V}}{\tilde{I}} = \frac{1}{i\omega C}$
- **Inductor** $\tilde{Z} = \frac{\tilde{V}}{\tilde{I}} = i\omega L$

Law 0.3.3. Generalized Voltage Divider is the complex version of the voltage divider formula that includes complex impedance.
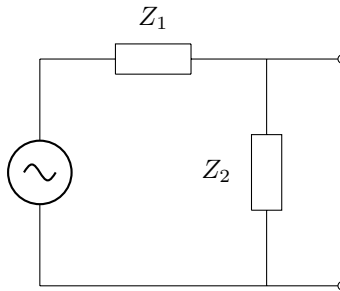
$$\tilde{V}_{out} = \tilde{V}_{in} \frac{\tilde{Z}_2}{\tilde{Z}_1 + \tilde{Z}_2}$$




0.3.1 AC Filters

Definition 0.3.5. A **Low Pass Filter** is a circuit that allows low frequency signals through, but blocks out higher frequency signals.

$$\tilde{V}_{out} = \tilde{V}_{in} \frac{1}{1 + i\omega RC}$$

$$V_{out} = V_{in} \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\phi = \tan(-\omega RC)$$

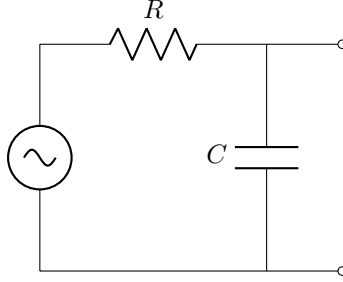


Definition 0.3.6. A **High Pass Filter** is a circuit that allows high frequency signals through, but blocks out lower frequency signals.

$$\tilde{V}_{out} = \tilde{V}_{in} \frac{1}{1 - \frac{i}{\omega RC}}$$

$$V_{out} = V_{in} \frac{1}{\sqrt{1 + (\frac{1}{\omega RC})^2}}$$

$$\phi = \tan(\frac{1}{\omega RC})$$

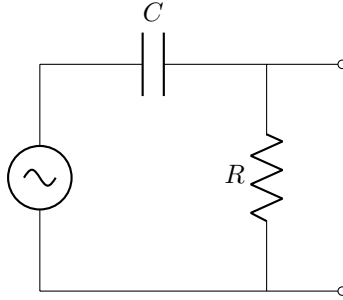

Definition 0.3.7. The **Breakpoint Frequency** is the frequency of a filter that produces an inflection point on the frequency response of that circuit. For simple low and high pass filters it can be represented as the following:

$$\omega_c = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi RC}$$

Definition 0.3.8. A **Decibel** scale is used to measure a ratio that can represent very large and very small values.


$$\text{Decibal} = 20 \log_{10}(|\frac{V_{out}}{V_{in}}|) = 10 \log_{10}(|\frac{P_{out}}{P_{in}}|)$$

Definition 0.3.9. A **Band Pass Filter** is a circuit that only allows mid range frequency signals through, but blocks out lower and higher frequency signals.

$$\tilde{V}_{out} = \tilde{V}_{in} \frac{1}{1 - \frac{i}{\omega RC} + i\omega L}$$

$$V_{out} = V_{in} \frac{1}{\sqrt{1 + (\omega \frac{L}{R} - \frac{1}{\omega RC})^2}}$$

$$\phi = \tan(\frac{1}{\omega RC} - \omega \frac{L}{R})$$

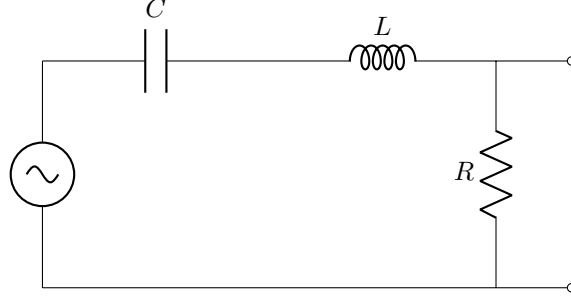

Definition 0.3.10. The **Resonance Frequency** is the frequency of resonance or max output for a band pass filter.

$$\omega_0 = \frac{1}{\sqrt{RL}}$$

$$f_0 = \frac{1}{2\pi\sqrt{RL}}$$

Definition 0.3.11. The **Band Width** is the difference between the two cutoff frequencies for a band pass filter.


$$\omega_{c1} - \omega_{c2} = \frac{R}{L}$$

$$f_{c1} - f_{c2} = \frac{R}{2\pi L}$$


Definition 0.3.12. The **Quality Factor** is a measure of the sharpness of the resonance peak of a band pass filter.

$$Q = \frac{f_0}{f_{c1} - f_{c2}} = \frac{\omega_0}{\omega_{c1} - \omega_{c2}}$$

Example. **Resonant High Pass Filter:**

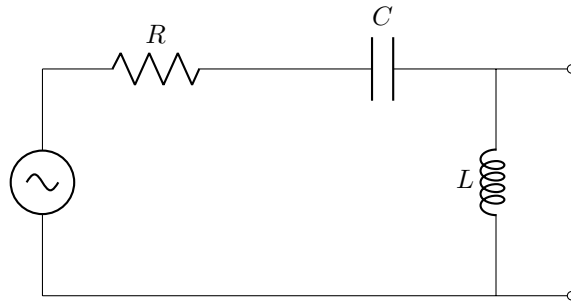

Example. Notch Filter:

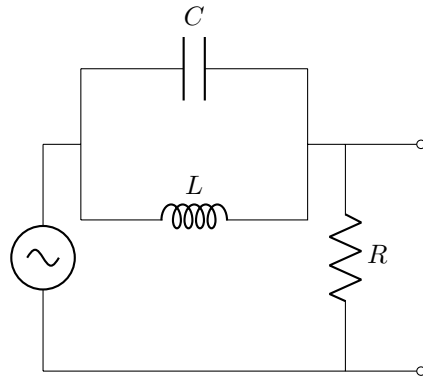


0.3.2 Transformers

Definition 0.3.13. A **Transformer** is a primary and secondary connected by a ferromagnetic core such that the primary coil induces voltage in the secondary.

$$\frac{V_S}{V_P} = \frac{N_S}{N_P}$$

$$\frac{I_S}{I_P} = \frac{N_P}{N_S}$$

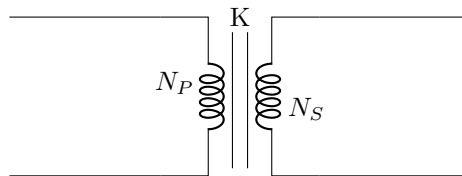

0.4 Silicon-based Components

Definition 0.4.1. **N-type silicon** is silicon doped with an element like Phosphorous which produces free electrons in the material.

Definition 0.4.2. **P-type silicon** is silicon doped with an element like Boron which produces electron holes in the material.

Definition 0.4.3. A **Diode(PN Junction)** is a device that has a very low resistance for current in one direction but a very high resistance for current in the other direction.

